

Formal verification

Verification of a timer

CERN training - July 2025

Context

We are interested in verifying the correctness of a timer having the following interface :


```
entity timer is
port (
  clk      : in  std_logic;
  rst      : in  std_logic;
  start    : in  std_logic;
  mode     : in  std_logic;
  value    : out std_logic_vector(7 downto 0);
  trigger  : out std_logic
);
end timer;
```

This timer is capable, from its start, of counting a certain number of cycles before generating a signal indicating its completion. The timer is started by activating the `start` signal for one clock cycle. When `start` is active, the `mode` input indicates the duration of the timer. If `mode` is set to '0', then the timer must count 6 cycles, and if it is set to '1', it must count 28 cycles. When `start` is activated, the timer begins decrementing until it reaches 0. When it reaches 0, the `trigger` output changes to '1' and remains so until the timer restarts (when `start` returns to '1').


The current value of the counter is also available as the `value` output.

The specifications of the timer state the the `start` input should not be activated before the timer is triggered.

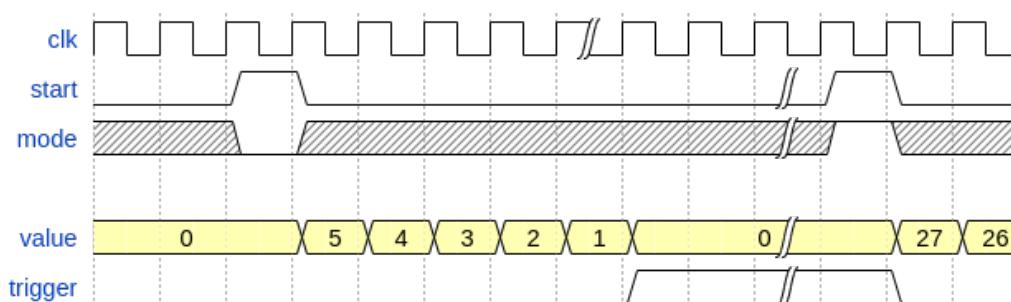The following waveform illustrates an example of how it works. The grayed-out mode indicates that the current value is not important.



 And the next one the minimum time between two activations of `start` :



Propose a set of assertions (and maybe assumptions) that allow you to use formal verification to prove the correct behavior of this timer. Make a good use of `assume` and `assert` to formally verify this timer.

The timer is able to generate errors, so you can test your assertions by changing the following statement in the `timer.sby` file :

`-gERRNO=0.`

ERRNO values :

- 0 : valid behavior
- in $[1, 5]$: wrong behavior